

I've merely made a PCB suitable for SMD components and tweaked the schematic/layout a bit so the circuit can be used both with a LDR or a photodiode as well as being able to be a led flasher for the start of the chain(s).

Video of the original on YouTube: <http://www.youtube.com/watch?v=PQ0jkuJtBfM>
Original project site: <http://relwin.hackhut.com/2011/03/01/555-timer-contest-entry/>

